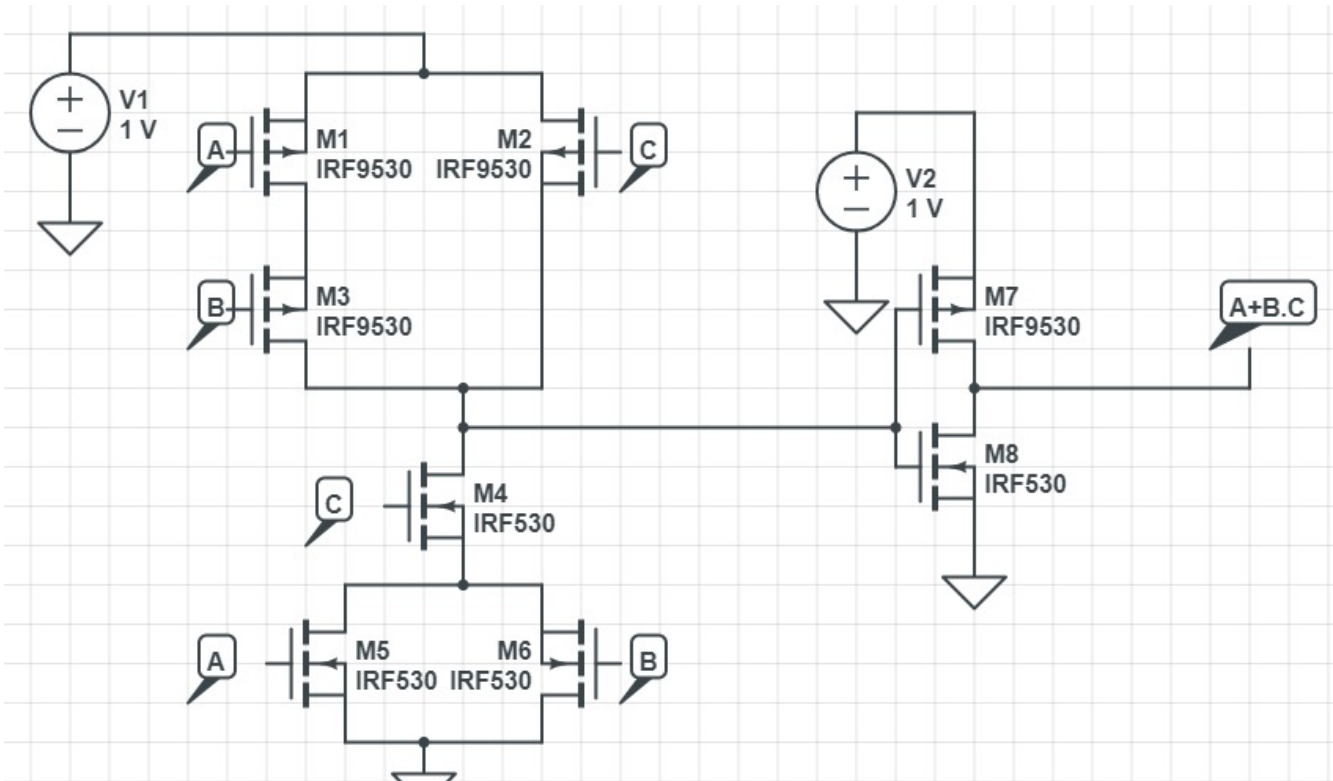


Task-8

Schematic of $Y=A+B.C$



Layout :

