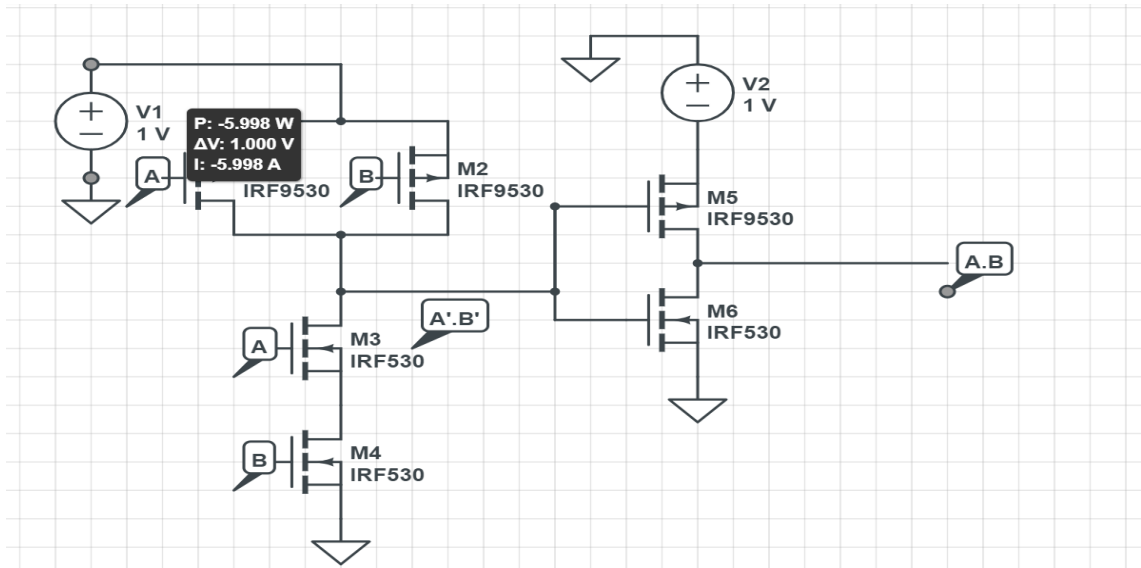


## Task-7

### Schematic of AND Gate



### Layout for AND Gate

