

TASK-02



FIG : BLOCK DIAGRAM OF FLIP FLOP

D	Q(Current)	Q(n+1) (Next)
0	0	0
0	1	0
1	0	1
1	1	1

FIG : TRUTH TABLE FOR D FLIP FLOP

CODE FOR D FLIP FLOP

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.STD_LOGIC_ARITH.ALL;
use IEEE.STD_LOGIC_UNSIGNED.ALL;
```

entity D_FLIPFLOP_SOURCE is

Port (D, CLK, RST : in STD_LOGIC;

Q, Qb : out STD_LOGIC);

end D_FLIPFLOP_SOURCE;

architecture Behavioral of D_FLIPFLOP_SOURCE is

begin

process (D, CLK, RST)

begin

if (RST = '1') then

Q <= '0';

elsif (rising_edge(CLK)) then ---this is for data flip-flop, for delay flip-flop use negative edge

Q <= D;

Qb <= not D;

end if;

end process;

end Behavioral;

TEST BENCH

library IEEE;

use IEEE.STD_LOGIC_1164.ALL;

use IEEE.STD_LOGIC_ARITH.ALL;

use IEEE.STD_LOGIC_UNSIGNED.ALL;

entity DFF_tb is

end entity;

architecture tb of DFF_tb is

component D_FLIPFLOP_SOURCE is

Port (D, CLK, RST : in STD_LOGIC;

Q, Qb : out STD_LOGIC);

end component ;

signal D, CLK, RST, Q, Qb : STD_LOGIC;

begin

uut: D_FLIPFLOP_SOURCE port map(

D => D,

CLK => CLK,

RST => RST,

Q => Q,

Qb => Qb);

Clock : process

begin

CLK <= '0';

wait for 10 ns;

CLK <= '1';

wait for 10 ns;

end process;

stim : process

begin

RST <= '0';

D <= '0';

wait for 40 ns;

D <= '1';

```
wait for 40 ns;
```

```
end process;
```

```
end tb;
```

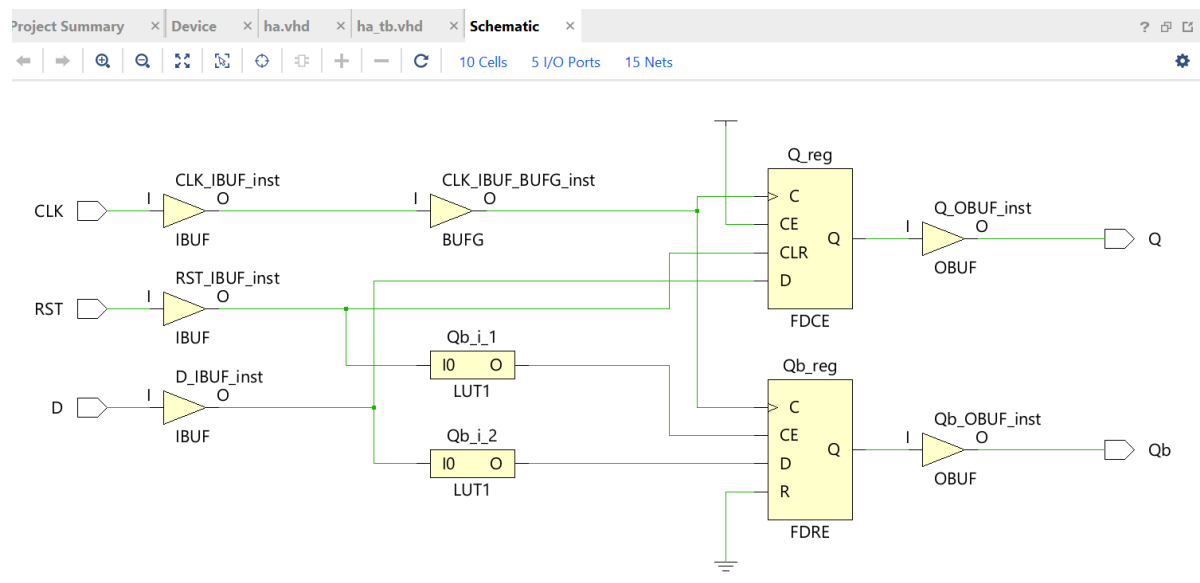


FIG : SCHEMATIC OF D FLIP FLOP

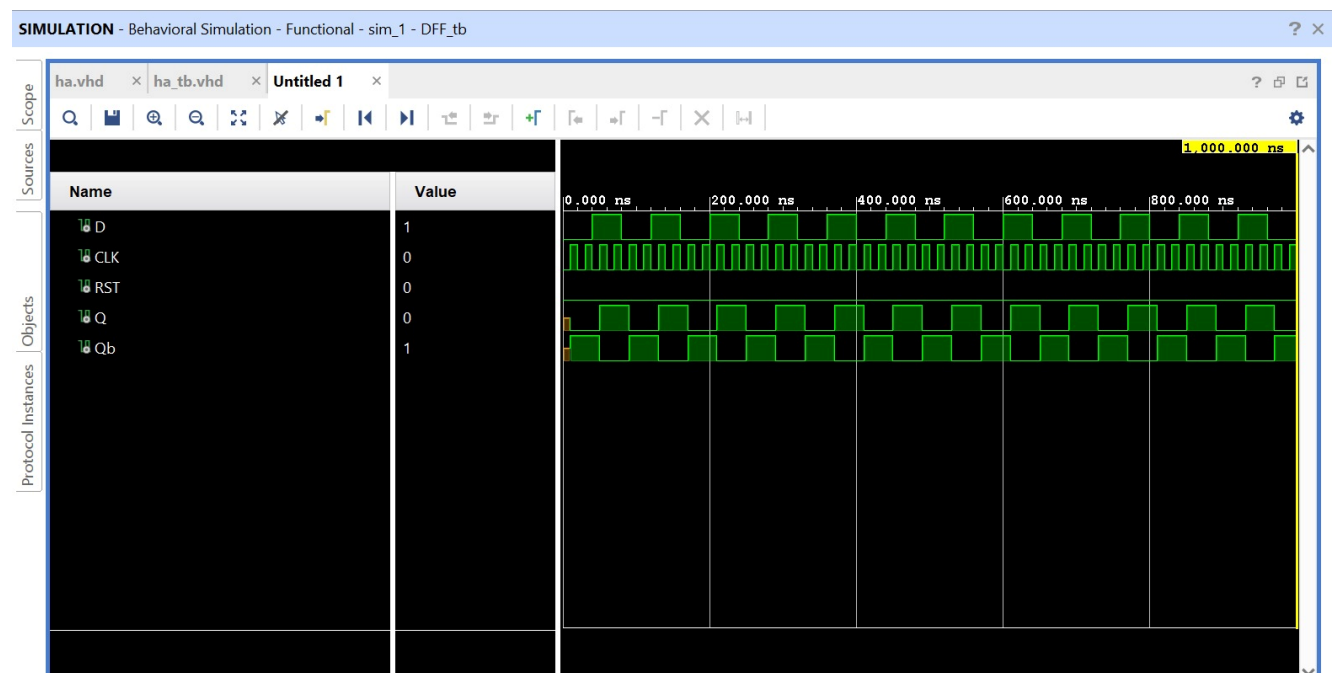


FIG : SIMULATION RESULT OF D FLIP FLOP

 


FIG: SYNTHESIS DESIGN